
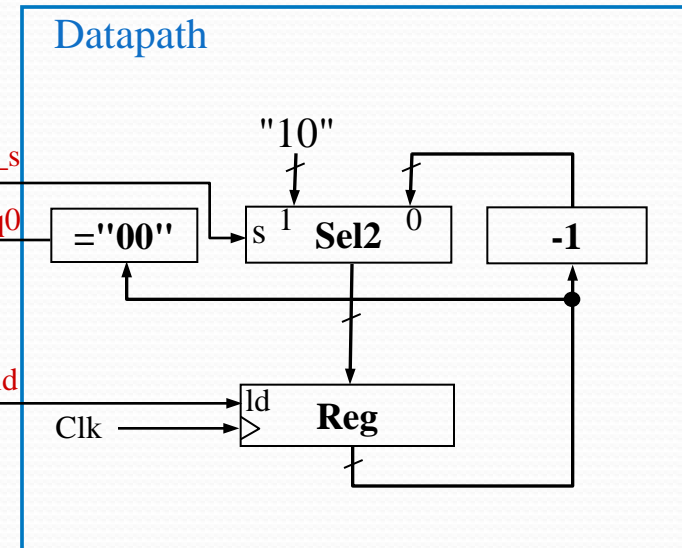
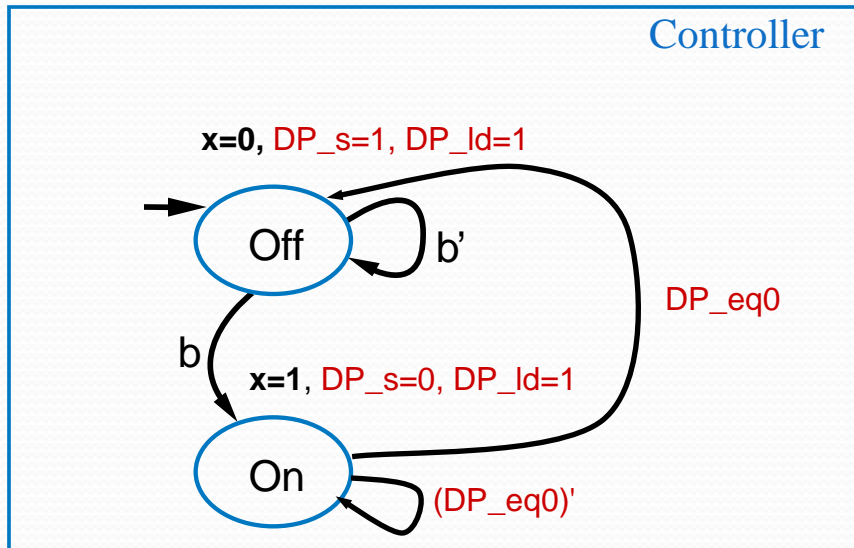
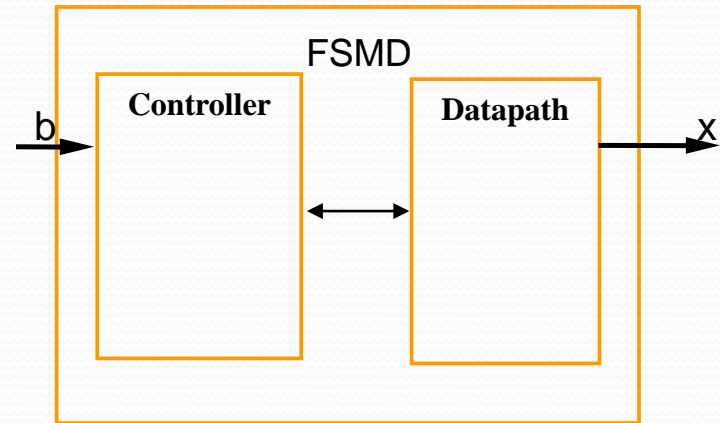


# FSMD Structure

 


# FSMD Controller
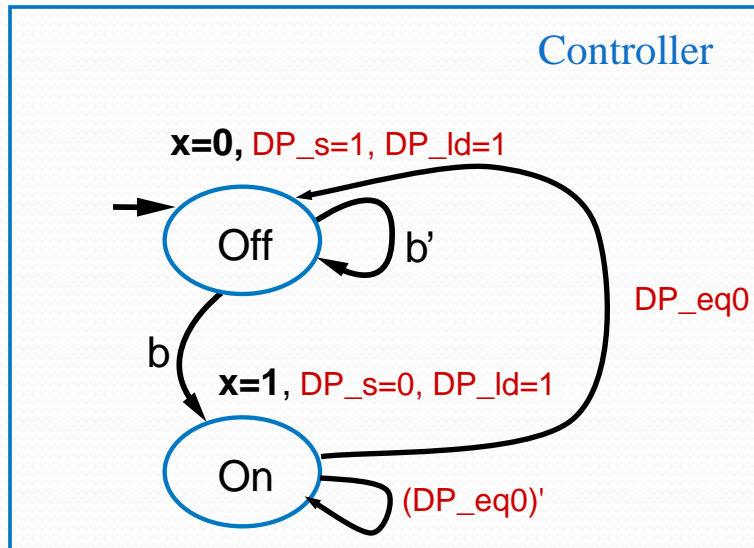
## Controller processes

```
CtrlLogic: PROCESS (Currstate, DP_eq0, b)
BEGIN
    CASE Currstate IS
        WHEN S_Off =>
            x <= '0'; DP_s <= '1'; DP_ld <= '1';
            IF (b = '0') THEN
                Nextstate <= S_Off;
            ELSE
                Nextstate <= S_On;
            END IF;
        WHEN S_On =>
            x <= '1'; DP_s <= '0'; DP_ld <= '1';
            IF (DP_eq0 = '1') THEN
                Nextstate <= S_Off;
            ELSE
                Nextstate <= S_On;
            END IF;
    END CASE;
END PROCESS CtrlLogic;
```

```
CtrlRegs: PROCESS (Clk)
BEGIN
    IF (Clk = '1' AND Clk'EVENT) THEN
        IF (Rst = '1') THEN
            Currstate <= S_Off;
        ELSE
            Currstate <= Nextstate;
        END IF;
    END IF;
END PROCESS CtrlRegs;
```



# FSMD Datapath

...


----- Datapath processes -----

```

DPLogic: PROCESS (DP_s, Reg)
BEGIN
  IF (DP_s = '1') THEN
    RegNext <= "10";
  ELSE
    RegNext <= Reg - "01";
  END IF;
  IF (Reg = "00") THEN
    DP_eq0 <= '1';
  ELSE
    DP_eq0 <= '0';
  END IF;
END PROCESS DPLogic;

DPRegs: PROCESS (Clk)
BEGIN
  IF (Clk = '1' AND Clk'EVENT) THEN
    IF (Rst = '1') THEN
      Reg <= "00";
    ELSIF (DP_ld = '1') THEN
      Reg <= RegNext;
    END IF;
  END IF;
END PROCESS DPRegs;
    
```

...

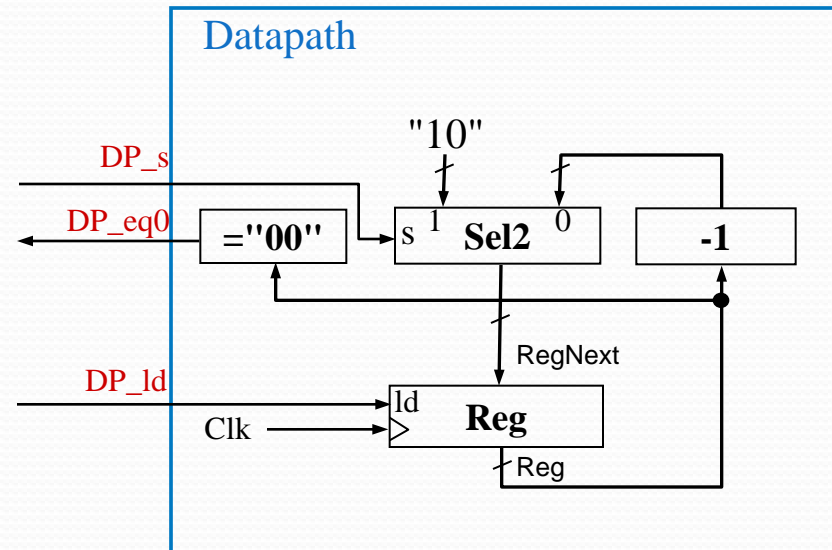

# 2-Bit Selector


```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY 2b_sel2 IS
    PORT (D0, D1: IN std_logic_vector (1 DOWNTO 0);
          s: IN std_logic;
          Y: OUT std_logic_vector (1 DOWNTO 0));
END 2b_sel2;

ARCHITECTURE 2b_sel2_beh OF sel2 IS
BEGIN

    PROCESS(D1, D0, s)
    BEGIN
        IF (s='0') THEN
            Y <= D0;
        ELSE
            Y <= D1;
        END IF;
    END PROCESS;

END 2b_sel2_beh;
```

 


# 2-Bit Register

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY 2b-Reg IS
    PORT (I: IN std_logic_vector(1 DOWNTO 0);
          Q: OUT std_logic_vector(1 DOWNTO 0);
          Ld, Clk, Rst: IN std_logic );
END 2b-Reg;

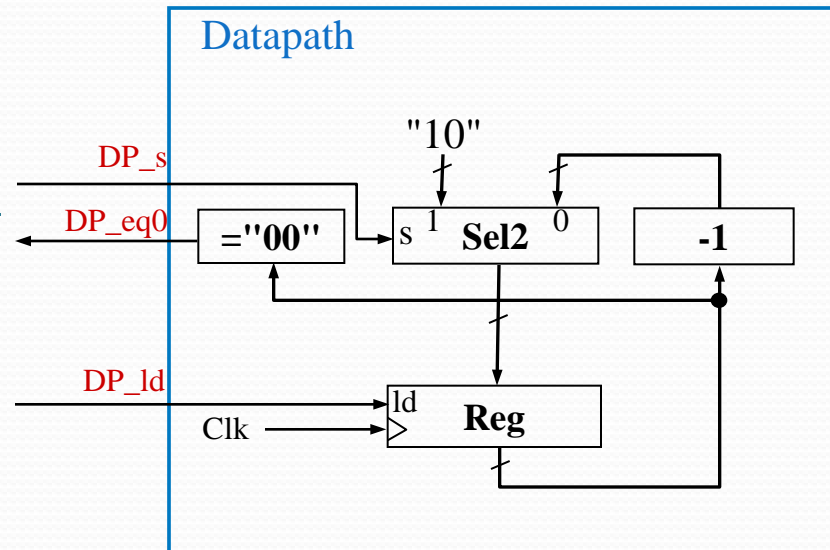ARCHITECTURE 2b-Reg_Beh OF 2b-Reg IS
BEGIN
    PROCESS (Clk)
    BEGIN
        IF (Clk = '1' AND Clk'EVENT) THEN
            IF (Rst = '1') THEN
                Q <= "00";
            ELSE IF (Ld = '1') THEN
                Q <= I;
            END IF;
        END IF;
    END PROCESS;
END 2b-Reg_Beh;
```




# 2-Bit Subtractor

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY 2b-Sub IS
    PORT (A, B: IN std_logic_vector(1 DOWNTO 0);
          S: OUT std_logic_vector(1 DOWNTO 0) );
END 2b-Sub;

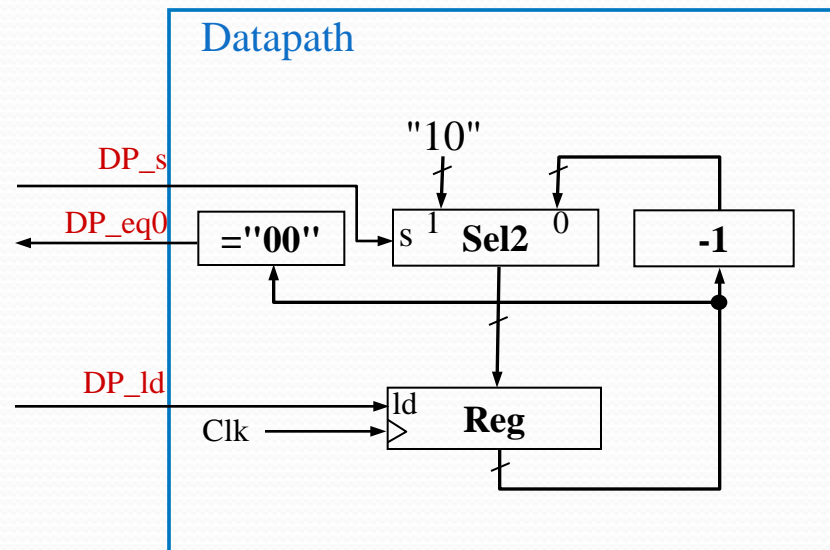ARCHITECTURE 2b-Sub_Beh OF 2b-Sub IS
BEGIN
    PROCESS (A, B)
    BEGIN
        S <= A - B;
    END PROCESS;
END 2b-Sub_Beh;
```




# 2-Bit Comparator


```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_arith.ALL;

ENTITY 2b-Comp IS
    PORT (A: IN unsigned(1 DOWNTO 0);
          B: IN unsigned(1 DOWNTO 0);
          Eq: OUT std_logic );
END 2b-Comp;

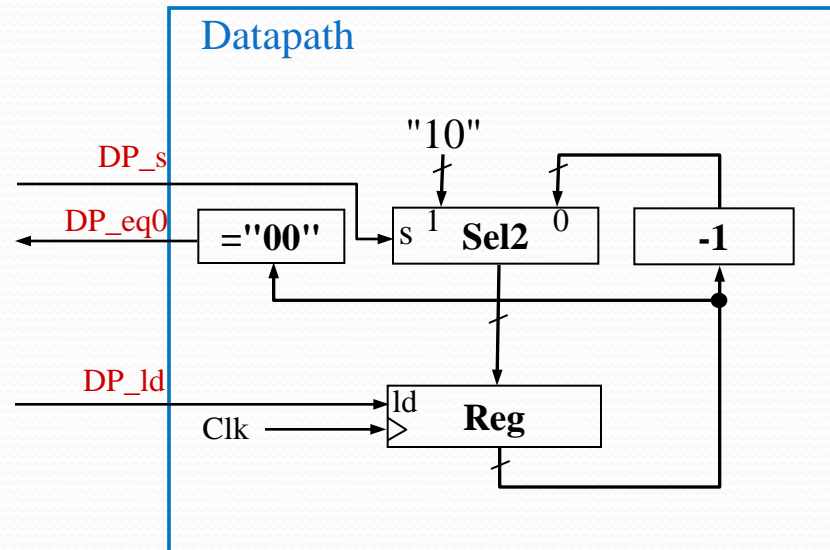ARCHITECTURE 2b-Comp_Beh OF 2b-Comp IS
BEGIN
    PROCESS (A, B)
    BEGIN
        IF (A = B) THEN
            Eq<='1';
        ELSE
            Eq<='0';
        END IF;
    END PROCESS;
END 2b-Comp_Beh;
```



# FSMD Structure

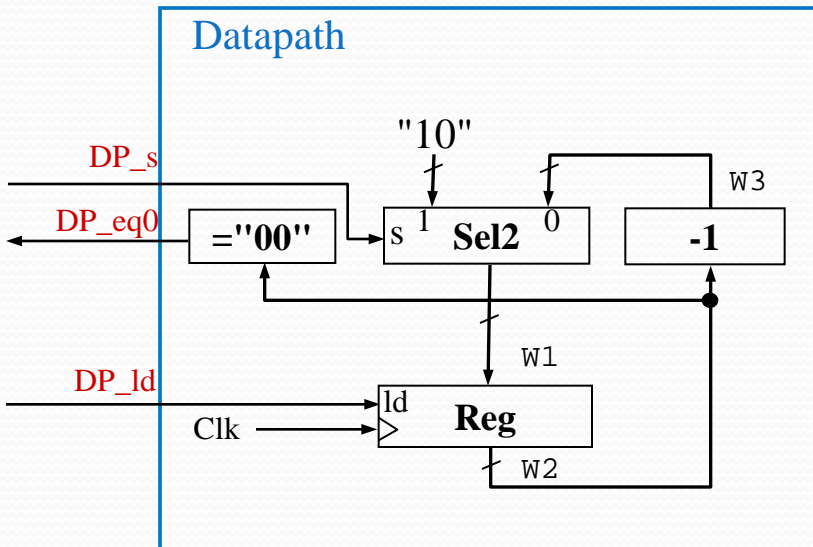

COMPONENT 2b-**Se12** IS

```
PORT (D0, D1: IN std_logic_vector(1 DOWNTO 0);
      Y: OUT std_logic_vector(1 DOWNTO 0);
      s: IN std_logic );
```

**END COMPONENT;**

COMPONENT 2b-Sub IS

```
PORT (A: IN std_logic_vector(1 DOWNTO 0);
      B: IN std_logic_vector(1 DOWNTO 0);
      S: OUT std_logic_vector (1 DOWNTO 0) );
```

**END COMPONENT;**

COMPONENT 2b-Reg IS

```

PORT (I: IN std_logic_vector(1 DOWNTO 0);
      Q: OUT std_logic_vector(1 DOWNTO 0);
      Ld: IN std_logic;
      Clk, Rst: IN std_logic );

```

**END COMPONENT;**

COMPONENT 2b\_Comp IS

```
PORT (A, B: IN unsigned (1 DOWNT0 0);
      Eq: OUT std_logic );
```

**END COMPONENT;**

```
SIGNAL W3, W2, W1: std_logic_vector(1 DOWNTO 0);
```

**BEGIN**

-----Controller-----

```
StateReg: 2b_Reg: PORT MAP (Nextstate, Currstate, "1",  
Clk, Rst);
```

```
CtrlLogic: PROCESS (Currstate, DP_eq0, b)
```

• • •

----- Datapath -----

```
Reg_1: 2b-Reg PORT MAP (W1, W2, DP_ld, Clk, Rst);
```

```
Sub_1: 2b-Sub PORT MAP ( W2, "01", W3);
```

```
Sel2_1: 2b-Sel PORT MAP (W3, "10", W1)
```

```
Comp_1: 2b-Comp PORT MAP (W3, "00", DP_Eq);
```

```
END Timer_Struct
```



# FSMD Behavior to Structure

